

## \* Chapter 1.

◇ Reading Assignment : 1.1., 1.2.,

### ◦ Electric Circuit (Electric Network)

- An interconnection of electrical elements linked together in a closed path so that an electrical current may flow continuously.

◦ Charge - the quantity of electricity responsible for electric phenomena.  
= 전하

② Current - the time rate of flow of electric charge past a given point.  
전하를 운반하는 속도가 아니다

◦ Direct current (dc current) - a current of constant magnitude.  
(not a function of time)

Let  $q$  = charge and  $i$  = current :  $i = \frac{dq}{dt}$  — ①

◦ Alternating current (ac current) : a sinusoidal time-varying current.  
간-단


from Eq. ① :  $q = \int_{-\infty}^t i d\tau = \int_0^t i d\tau + q(0)$   
dummy note:  $\int \tau d\tau$

where :  $q(0)$  = the charge at  $t=0$ .

### ② Voltage

- The voltage across an element is the work (energy) required to move a unit "positive" charge from the '-' terminal to the '+' terminal. (The unit = V)  $= \Delta W$

$$V = \frac{dW}{dq}$$

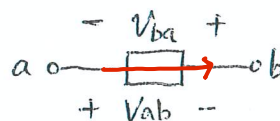

$$V_{ab} = -V_{ba}$$

Eq.) A charge of 1 coulomb delivered an energy of 1 joule as it moves through a voltage of 1 volt.

Note)

Energy (W) = the capacity to perform work.  
= Work

## ◆ Power and Energy

• Power = the time rate of expending or absorbing energy.

(P)

$$P = \frac{dW}{dt} \quad [\text{watts}]$$

(-) : 소비

(+) : 공급

부호 기호 : 전기가 "공급" (+) 같아


- The power associated with the current flow through an element

$$P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = \underline{v \cdot i}$$

(Note) Power absorbed or supplied by an element

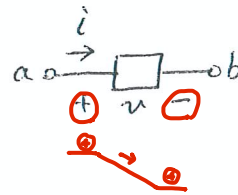1) Power absorbed by an element


Since the reference direction of  $v$  and  $i$  adhere to the passive convention, the power  $P = vi$  is the power absorbed by the element.



부호 기호 : 전기가 맞았기 막다

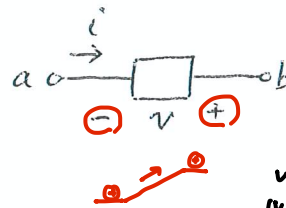2) Power supplied by an element

Since the reference direction of  $v$  and  $i$  do not adhere to the passive convention, the power  $P = vi$  is the power supplied by the element.



∴ power absorbed = - power supplied


• The energy absorbed by an element

$$dW = P \cdot (dt)$$

$$W = \int_{-w}^t P d\tau$$

If the element only receives power for  $t \geq t_0$  and let  $t_0 = 0$ , then

$$W = \int_0^t P d\tau$$

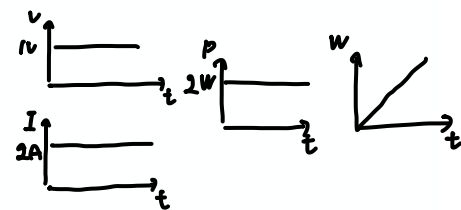

공급기가 생각나는 공격한 시간